 




تصميم الدارات الإلكترونية بالحاسوب



Computer Design of Electronic Circuits



إعداد: د. علا جزماتي

السنة الرابعة قسم التحكم والأتمتة
العام الدراسي 2023-2024

المحاضرة الثالثة

محتويات المقرر

1. مدخل إلى أهمية تطوير أدوات التصميم باستخدام الحاسب (Introduction to The Need of Developing CAD Tools)
2. تصنيف عام لأنواع أدوات التصميم (General Classification of CAD Tools Used in Electronic Systems Design)
3. مدخل إلى اللغات المستخدمة في التصميم (..) (Introduction to Design Languages VHDL, Verilog, Verilog System, ..)
4. مدخل إلى مراحل بناء النظم الرقمية (Introduction to Digital Systems Synthesis)
5. مرحلة البناء منخفض المستوى (Low Level Synthesis)
6. تصميم الدارات المتكاملة للنظم عالية التكامل (Layout Design for VLSI Systems)
7. تطبيقات تصميمية (Design Applications)
8. اتجاهات التطور الحديثة (Trends and New Directions)

تطبيقات حول التوصيف البنيوي:

// Half adder

```
module halfadder(  
    input a,  
    input b,  
    output o,  
    output c  
);
```

```
    assign o = a ^ b;  
    assign c = a & b;
```

```
endmodule
```

// Full adder


```
module fulladder(  
    input a,  
    input b,  
    input d,  
    output o,  
    output c  
);
```

```
    wire t, c1, c2;
```

```
    halfadder ha1(a, b, t, c1);  
    halfadder ha2(t, d, o, c2);
```

```
    assign c = c1 | c2;
```

```
endmodule
```

 

توصيف بنيوي لإدارة Full Adder :

```
module full_adder_4b ( input [3:0] a, input [3:0] b, input cin, output [3:0] sum, output cout );  
wire [4:0] c;  
wire [3:0] s;  
genvar i;  
generate for (i = 0; i < 4; i = i + 1)  
begin :  
label full_adder fa (a[i], b[i], c[i], s[i], c[i+1]);  
end  
endgenerate  
assign sum = s;  
assign cout = c[4];  
assign c[0] = cin ;  
endmodule
```

```
module full_adder ( input a, input b, input  
cin, output sum, output cout );  
  
assign sum = a ^ b ^ cin;  
assign cout = (a & b) | (a & cin) | (b & cin);  
  
endmodule
```

حاول توصيف هذا النظام
بطريقة أخرى وارسم
المخطط الصندوقي له

توصيف بنيوي لدارة Full Adder :

ملاحظات:

- يتم استخدام الأمر **generate** لإنشاء مجموعة من كائنات **full_adder**، حيث يتم إنشاء عدد من الكائنات يساوي عدد البتات (4 في هذا المثال)، وكل كائن يستخدم **Full Adder** لجمع البتات المقابلة في **a** و **b** و **c**.
- يتم توصيل الحمل الناتج من الكائن السابق إلى الكائن التالي بواسطة إشارة **c[i+1]**.
- يتم استخدام الأمر **assign** لإسناد قيمة الإشارات **sum** و **cout** إلى الإشارات الوسيطة **s** و **c[4]** على التوالي.
- **genvar** هي كلمة مفتاحية في لغة **Verilog** وهي اختصار لـ **generate variable** تستخدم لتعريف متغيرات تستخدم في الأوامر المرتبطة بالأمر **generate**، مثل **for loops** و **if statements**. يمكن استخدام **genvar** لتحديد متغير يتم تكرار قيمه في كل مرة يتم فيها تكرار الأمر المرتبط به، مثل إنشاء مجموعة من الكائنات. يمكن استخدام **genvar** في أي مكان داخل الأوامر المرتبطة بالأمر **generate**، ويجب تعيين قيمة ابتدائية للمتغير قبل استخدامه.



7762



Setup

I/O

fulladder.sv



```
12 endmodule
```

```
13
```

```
14 // Full adder
```

```
15 module fulladder(
```

```
16   input a,
```

```
17   input b,
```

```
18   input d,
```

```
19   output o,
```

```
20   output c
```

```
21 );
```

```
22
```


```
23 wire t, c1, c2;
```

```
24
```

```
25   halfadder ha1(a, b, t, c1);
```

```
26   halfadder ha2(t, d, o, c2);
```

Synthesize and simulate!
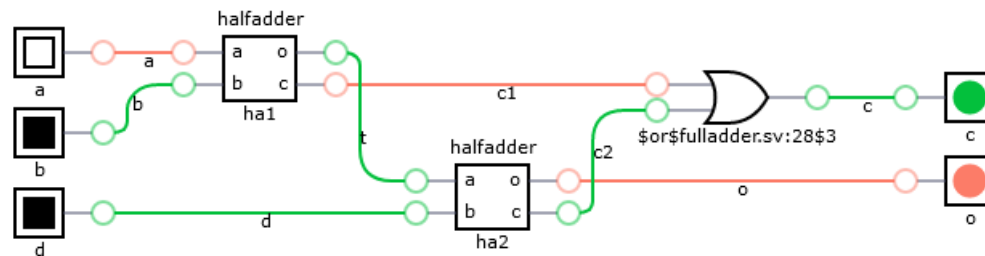
<http://digitaljs.tilk.eu/#>

+

-

scale

2



range

7566



7762


o



Setup I/O fulladder0.sv

```
1 // Half adder
2 module halfadder(
3     input a,
4     input b,
5     output o,
6     output c
7 );
8
9     assign o = a ^ b;
10    assign c = a & b;
11
12 endmodule
13
14 // Full adder
15 module fulladder(
16     input a,
17     input b,
18     input d,
19     output o,
20     output c
21 );
```

Synthesize and simulate!

 

On Line

<http://digitaljs.tilk.eu/#>



Setup I/O fulladder.sv


DigitalJS Online

This is a demonstration app for the [DigitalJS](#) digital logic simulator and the [yosys2digitaljs](#) netlist format converter, by [Marek Materzok](#), [University of Wrocław](#). The source files [are on Github](#). Contributions are welcome! This was made possible by the [Yosys](#) open-source hardware synthesis framework.

Create a new tab and enter your SystemVerilog code, or load an example by using the dropdown menu, and press the Synthesize button to start the simulation.

Drop your files here or click for a file dialog

Additional SystemVerilog files:

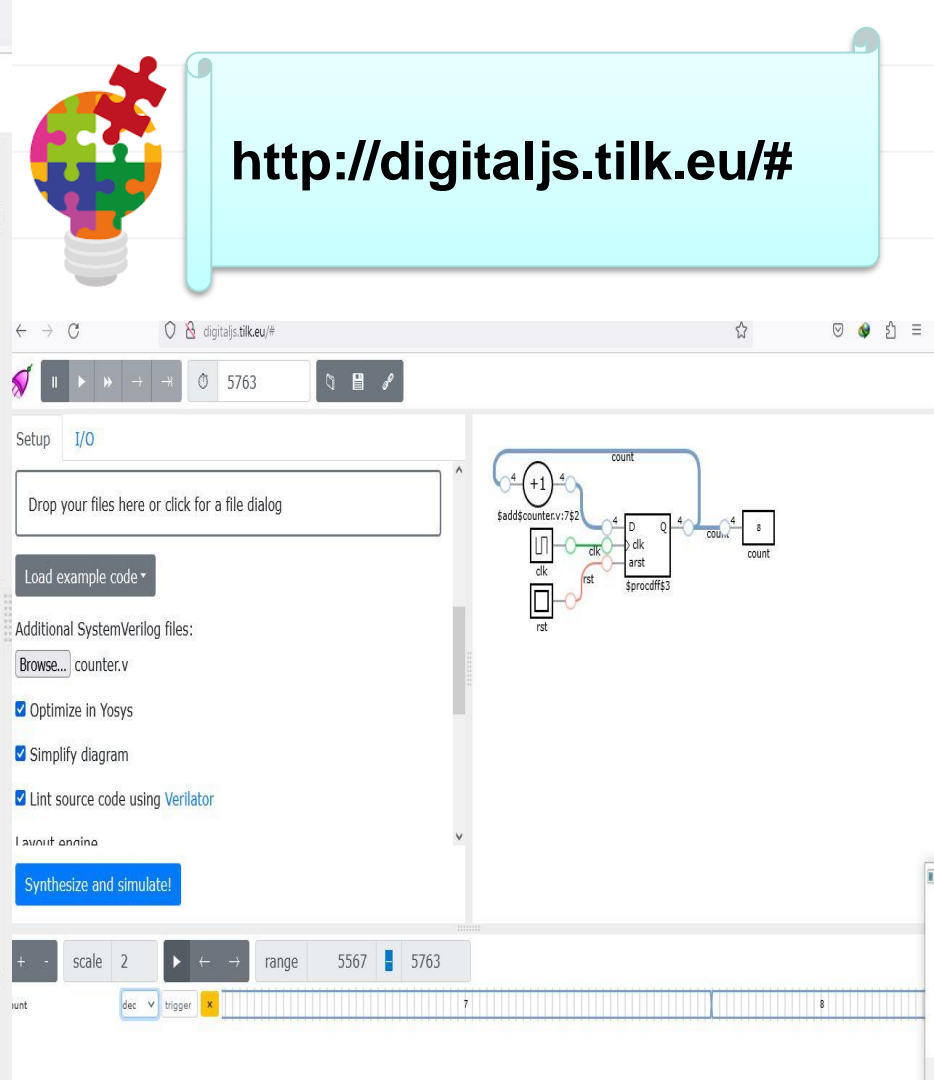

always

► **Basic syntax:**

Signal list - change activates block

always (*sensitivity-list*)

statement \longleftarrow Sequential statement (=, if/else, etc.)

or


always (*sensitivity-list*)

begin

statement-sequence

Compound Statement - sequence of sequential statements

end

 

initial


Syntax



```
1 initial  
2   [single statement]
```


 
```
4 initial begin  
5   [multiple statements]  
6 end
```



Delays in Behavioral Verilog

- Blocking Delay

▶ Delay control statement -

`#n sequential_statement`

- ▶ Simulation effect: suspends simulation for n time units before simulating following statement

▶ Example: clock generator

```
always
begin
    clk = 0;
    #50 clk = 1;
    #50 ;
end
```


← null statement
(suspends simulation 50 time units)



Delays in Behavioral Verilog

- Blocking Delay
 
```
initial x = 0;  
initial begin  
    #25 x = 1;  
    #10 x = 0;  
    #5;  
end
```



Simulation Time in Verilog:

``timescale`

- ▶ ``timescale` controls simulation time

```
`timescale time_unit time_precision
```

```
`timescale 1ns 100ps
```

- ▶ `#` operator specifies delay in terms of time units

```
`timescale 1ns 100ps
```


```
#5      // delays 5*1ns = 5ns;
```

```
`timescale 4ns 1ns
```

```
#3      // delays 3*4ns = 12ns
```

Simulation Time in Verilog:


`timescale

 

Character	Unit
s	seconds
ms	milliseconds
us	microseconds
ns	nanoseconds
ps	picoseconds
fs	femtoseconds

Verilog code for and_gate
 
```
module and_gate(input a, input b, output y);  
    assign y = a & b;  
endmodule
```




Verilog Testbench code to simulate and_gate

```
module test ();  
    reg a1, b1;  
    wire y1;  
    and_gate uut ( .a(a1), .b(b1), .y(y1) );  
    Initial begin  
        a1 = 0; b1 = 0;  
        #10 a1 = 0; b1 = 1;  
        #10 a1 = 1; b1 = 0;  
        #10 a1 = 1; b1 = 1;  
    end endmodule
```

Verilog code for Rising Edge D Flip Flop
 
```
module d_flip_flop(input d, input clk, output reg q);  
  always @(posedge clk)  
  begin  
    q <= d;  
  end  
endmodule
```





Design

↔ □ ✕

View: ☒ Implementation ☐ Simulation

Hierarchy

- Test1
 - xc3s700an-5fgg484
 - d_flip_flop (d_flip_flop.v)



No Processes Running

Processes: d_flip_flop

- Design Summary/Reports
- Design Utilities
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simulation Model
- Implement Design
 - Generate Programming File
 - Configure Target Device
 - Analyze Design Using ChipScope

Start Design Files Libraries

```
1 `timescale 1ns / 1ps
2 //////////////////////////////////////
3 // Additional Comments:
4 //
5 //////////////////////////////////////
6 module d_flip_flop(input d, input clk, output reg q);
7 always @(posedge clk)
8 begin
9     q <= d;
10 end
11 endmodule
12
13
```

**AMD**
XILINX

d_flip_flop.v*

Design Summary (Synthesized)



Design View: Implementation Simulation


Hierarchy

- Test1
 - xc3s700an-5fgg484
 - d_flip_flop (d_flip_flop.v)

No Processes Running

Processes: d_flip_flop

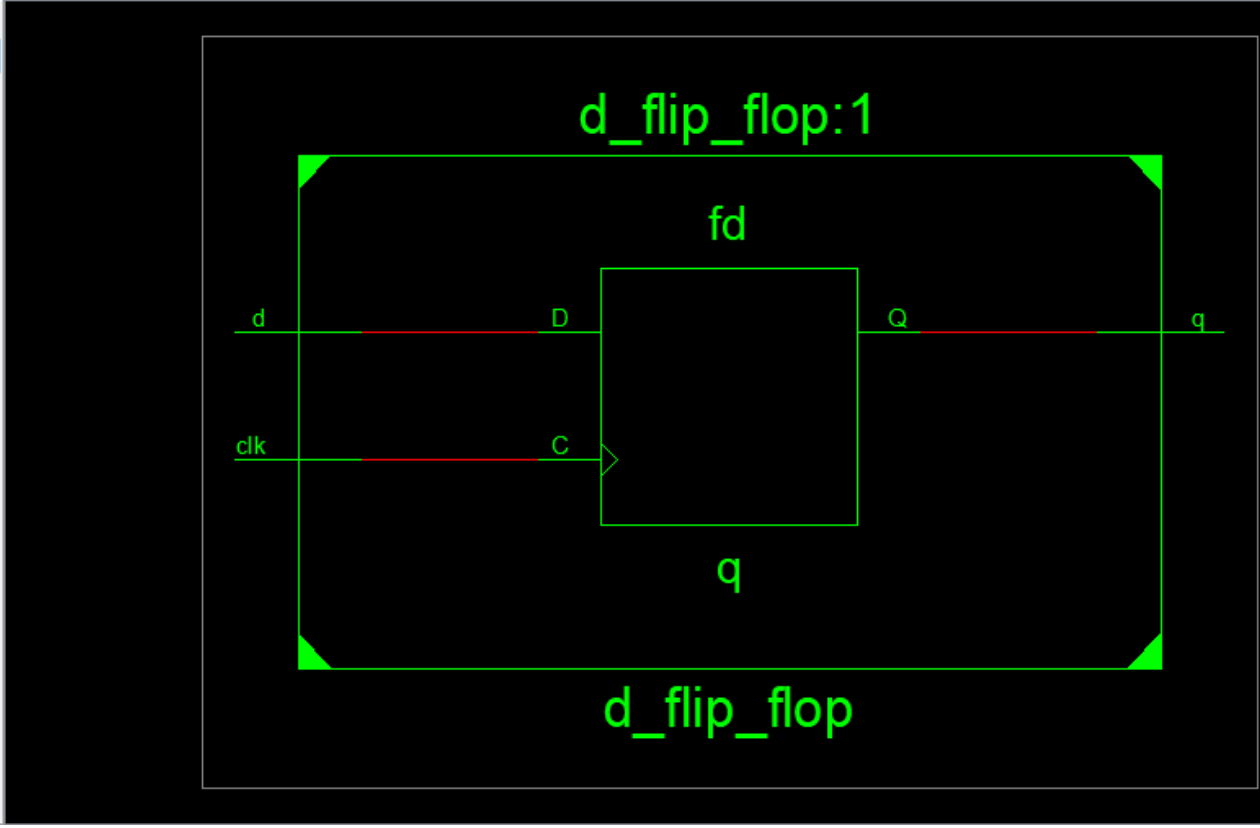- Design Summary/Reports
- Design Utilities
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simulation Model
- Implement Design
 - Generate Programming File
 - Configure Target Device
 - Analyze Design Using ChipScope



Verilog Testbench code to simulate D Flip-Flop:

ISE Project Navigator (P.58f) - D:\Users\USER\Desktop\Test1\Test1.xise - [tset.v]

The screenshot displays the ISE Project Navigator interface with the following components:

- Menu Bar:** File, Edit, View, Project, Source, Process, Tools, Window, Layout, Help.
- Toolbar:** Standard ISE icons for file operations, simulation, and project management.
- Design Panel:** Shows the project hierarchy under 'Test1'. The selected item is 'test (tset.v)', which contains a sub-entity ' uut - d_flip_flop (d_flip_flop.v)'. The 'Simulation' view is active.
- Processes Panel:** Shows the simulation process 'test' with the 'Simulate Behavioral Model' option selected.
- Code Editor:** Contains the Verilog testbench code for the D Flip-Flop simulation.


The Verilog code in the editor is as follows:

```
1  `timescale 1ns / 1ps
2  module test;
3
4      // Inputs
5      reg d;
6      reg clk;
7
8      // Outputs
9      wire q;
10
11     // Instantiate the Unit Under Test (UUT)
12     d_flip_flop uut ( d, clk, q);
13     always #5 clk = ~clk;
14
15     initial begin
16         // Initialize Inputs
17         d = 0;
18         clk = 0;
19         #10 d = 1;
20         #20 d = 0;
21         #30 d = 1;
22     end
23
24 endmodule
```

Hand-drawn annotations highlight specific sections of the code:

- A yellow bracket groups lines 4 through 9, covering the input and output declarations.
- A red bracket groups lines 15 through 22, covering the initial conditions and input sequence.

 Verilog Testbench code to simulate D Flip-Flop:



Verilog code for up counter

```
module up_counter(input clk, reset, output[3:0] counter);  
  reg [3:0] counter_up;  
  // up counter  
  always @(posedge clk or posedge reset)  
  begin  
    if(reset)  
      counter_up <= 4'b0;  
    else  
      counter_up <= counter_up + 4'b0001;  
    end  
  assign counter = counter_up;  
endmodule
```


Verilog code for up counter test

```
module upcounter_testbench;
    // Inputs
    reg clk;
    reg reset;
    // Outputs
    wire [3:0] counter;
    // Instantiate the Unit Under Test (UUT)
    up_counter uut (
        .clk(clk),
        .reset(reset),
        .counter(counter) );
    always #5 clk=~clk;
    initial begin
        // Initialize Inputs
        clk = 0;
        reset=1;
        #10;
        reset=0;
        #10;
    end
endmodule
```

Or

up_counter uut (clk, reset, counter)

Verilog code for up counter test

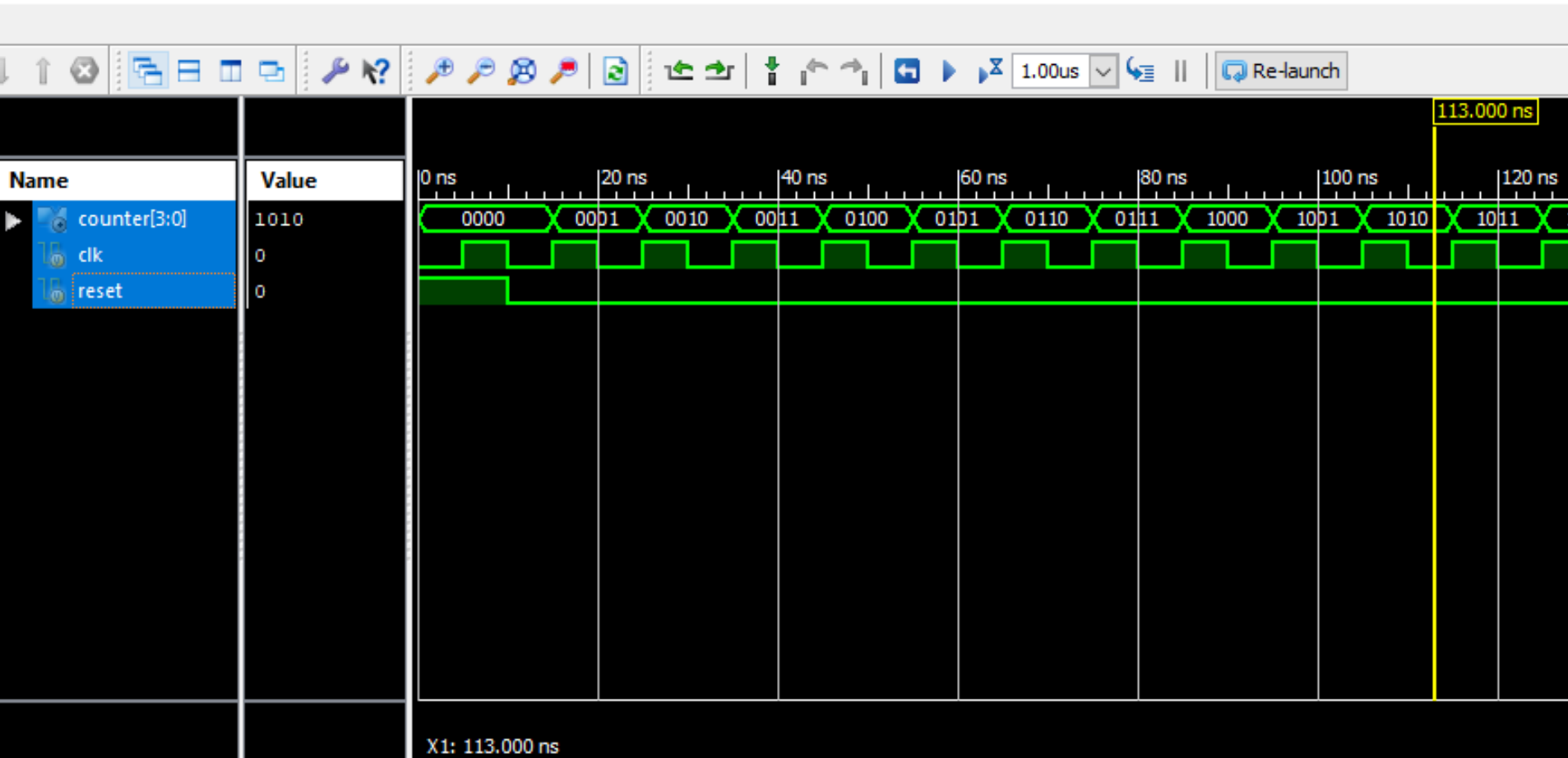



الأسئلة والمناقشة

